
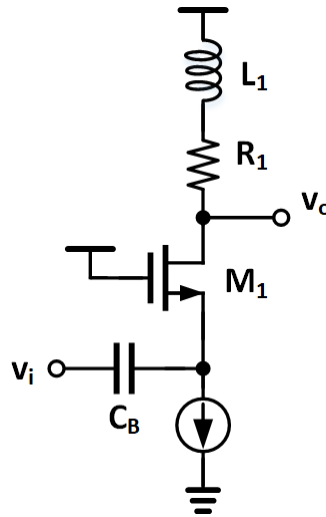


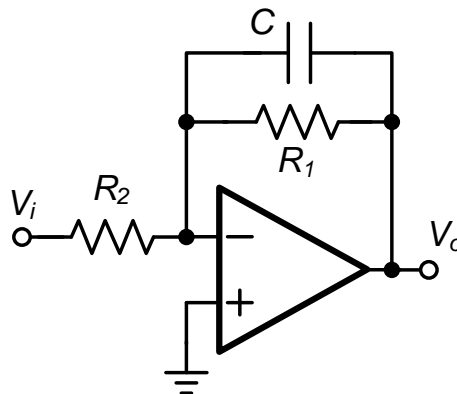
1. [15 pts] The circuit under analysis is as shown as in the following figure.  $M_1$  is not ideal. That is, there exist  $C_{gs}$ ,  $C_{gd}$ , and transistor output resistance  $r_o$ . Let  $C_B$  be an ideal dc block at the input. Assume  $\omega L_1/R_1 > 3$ .
- What is the frequency when the maximum voltage gain occurs?
  - Formulate and find out the value of the maximum voltage gain,  $v_o/v_i$ .




2. [10 pts] Assume the operational amplifier is ideal. Design the circuit such that the input impedance is  $500\ \Omega$ , voltage gain is 20 dB, and the frequency of unity gain is at 2000 rad/sec.



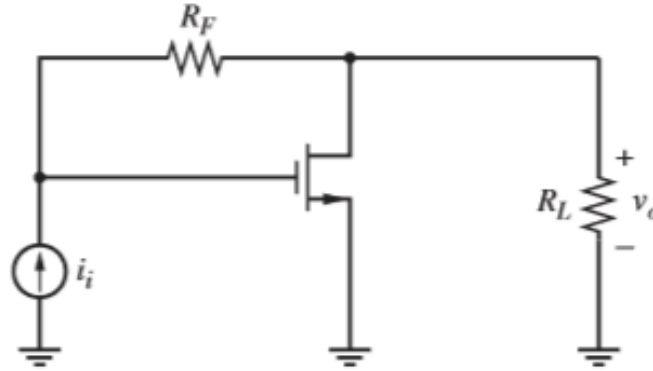
3. [10 pts] Consider an ac schematic of a local shunt-shunt feedback circuit shown below. For the MOS transistor,  $I_D = 0.5\text{mA}$ ,  $W/L = 100$ ,  $k' = 200 \mu\text{A/V}^2$ , and  $r_o = \infty$ . If  $R_F = 200\text{k}\Omega$ , and  $R_L = 50\text{k}\Omega$ . Please calculate input resistance, out resistance, loop transmission, and close-loop gain.




4. [15 pts] A voltage-follower feedback circuit is shown below. For the MOS transistor,  $I_D = 0.5\text{mA}$ ,  $k' = 180 \mu\text{A/V}^2$ ,  $r_o = \infty$ ,  $W/L = 100$ ,  $|\phi_t| = 0.3\text{V}$ , and  $\gamma = 0.3\text{V}^{1/2}$ . For the op amp, assume that the input resistance  $R_i = 1\text{M}\Omega$ , the output resistance  $R_o = 10\text{k}\Omega$ , and the voltage gain  $a_v = 1,000$ . Please calculate input resistance, output resistance, loop transmission, and closed-loop gain:

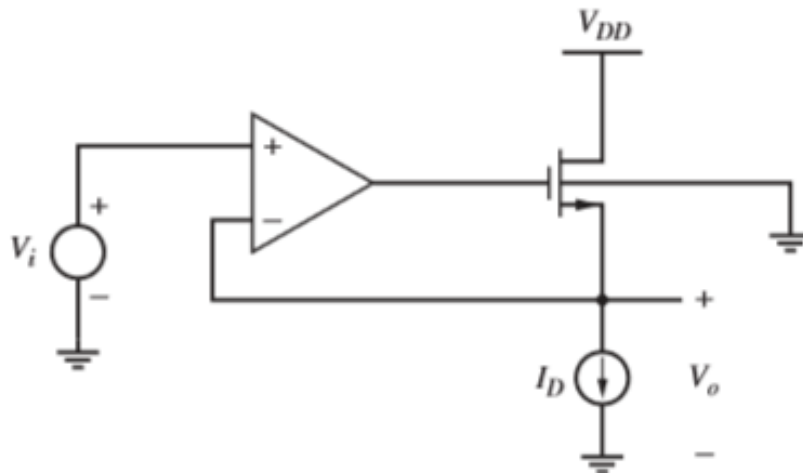

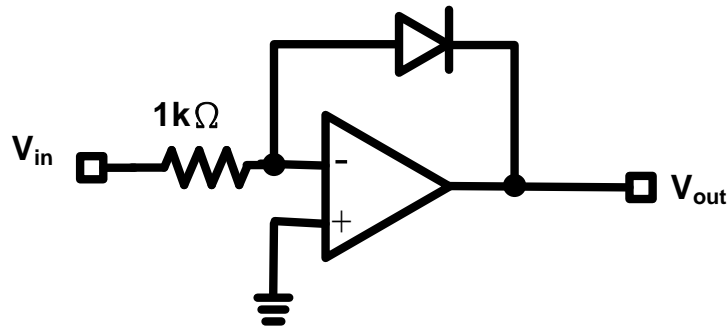5. [15 pts] In the schematic shown below, assume the operational amplifier is ideal. The diode has a I-V curve of:  $I_D = I_s \left( e^{\frac{V_D}{V_T}} - 1 \right)$ , with  $V_T = 25mV$  and  $I_s = 1nA$ . The diode has a reverse breakdown voltage of 10 V.
- Please plot the relationship between  $V_{out}$  and  $V_{in}$ . You will need to provide your calculation process.
  - What is the output voltage  $V_{out}$  when  $V_{in} = 1V$ .
  - Can you identify the range of  $V_{in}$  that the diode will be damaged?



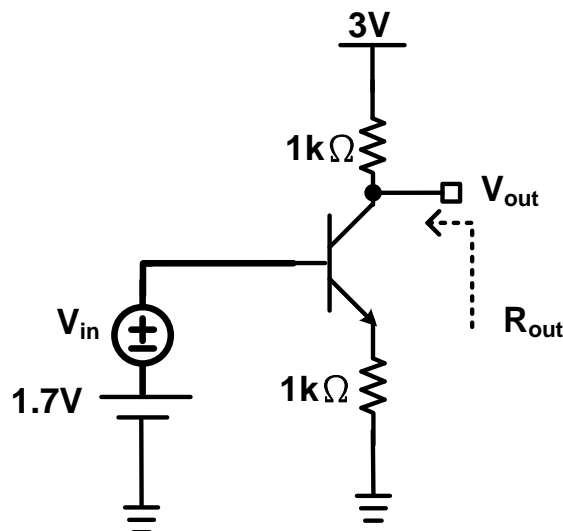
6. [10 pts] For the amplifier shown below,  $V_{in}$  is assumed to be a small signal source. The BJT has  $\beta = 100$ , and  $V_A = 20V$ . Ignore all parasitic capacitance, and assume  $25mV$  thermal voltage.
- What is the small signal gain ( $V_{out}/V_{in}$ )?
  - What is the output resistance ( $R_{out}$ )?



☐ 可看書 ☒ 不可看書 (可帶計算器但僅限四則運算者)

考試日期：107 年 8 月 7、8 日

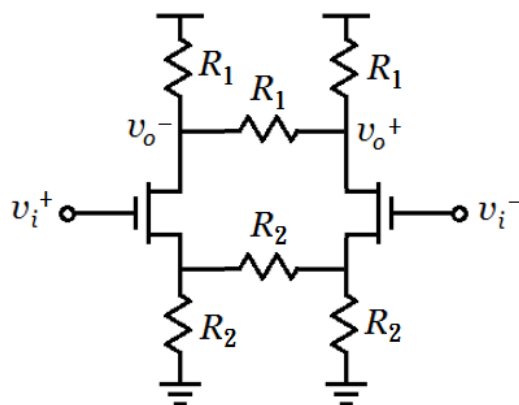7. [10 pts] Consider the differential amplifier shown below. Assume that all the transistors are biased in the saturation region. Neglect the body effect and the channel-length modulation effect. Let  $g_m = 1 \text{ mA/V}$ ,  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ . Find the common-mode-rejection ratio CMRR.



8. [15 pts] Consider the differential amplifier shown below. Assume that all the transistors are biased in the saturation region. Neglect the body effect. Let  $g_m = 1 \text{ mA/V}$ ,  $r_o = 20 \text{ k}\Omega$  for all the transistors.
- Find the output resistance of the amplifier.
  - Find the small-signal gain of the amplifier  $v_o / (v_i^+ - v_i^-)$ .

